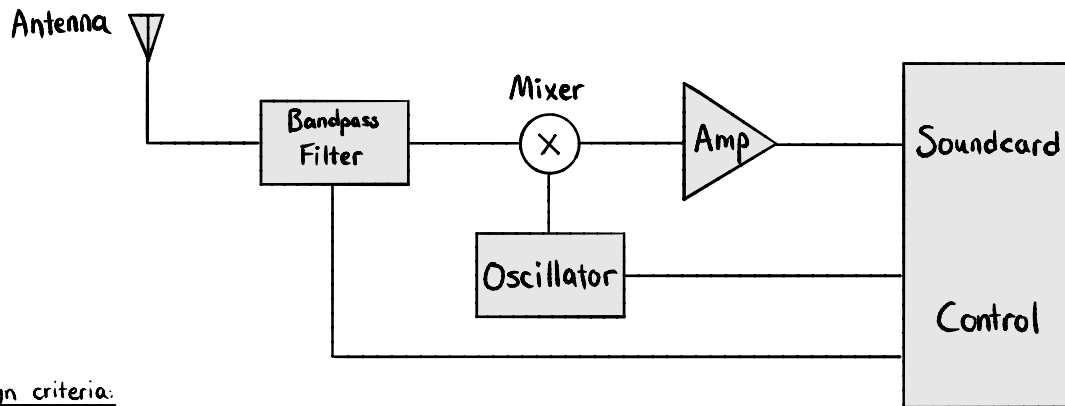


Basic block diagram of SDR receiver:



Our design criteria:

Bandpass Filter: (Butterworth)

- only pass 5-10MHz.
- butterworth (not as sensitive)

Oscillator:



- Use clock generator controlled by Arduino v3.
- SI5351 A-B-GT (\$0.92 Digikey) *needs 25, 27 MHz crystal*
- 4x as fast as RF frequency.
- Divide with Johnson Counter. (see below)

Intermediate Frequency:

- standard 10.7kHz

Image Reject Mixer: (Taylor Mixer)

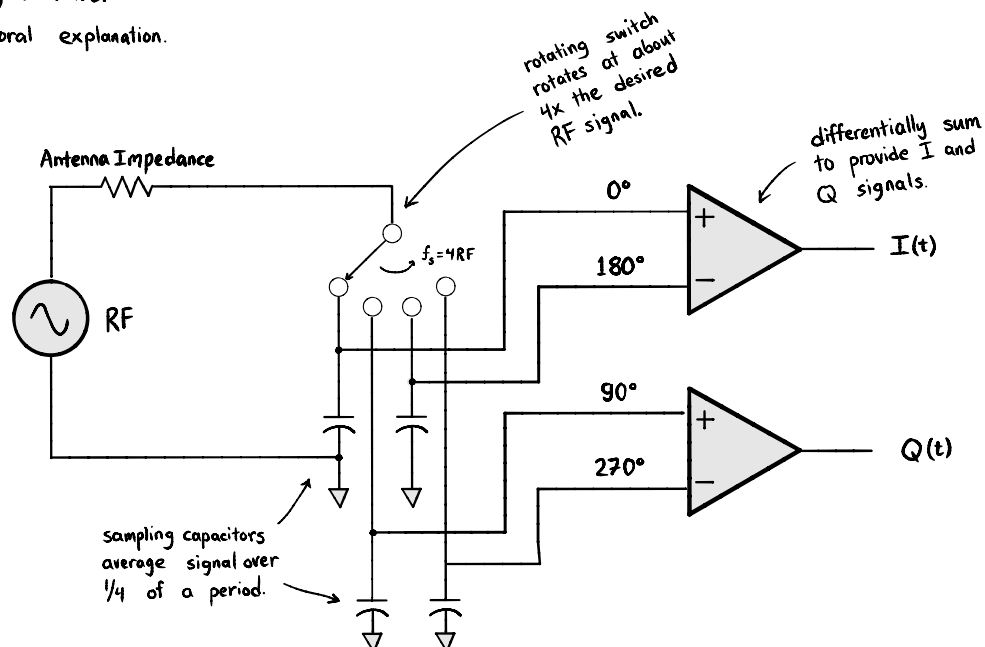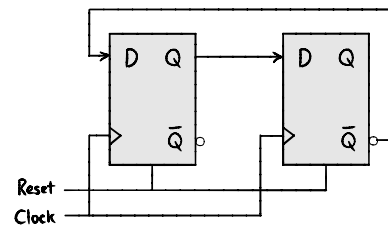- generate quadrature signals that are 90°
- Taylor mixer works by sampling the signal 4x a period. Capacitors are used to average the signal value.
- See below for pictorial explanation.



Receiver Design - Block Diagram

